

# **UART RECEIVER – PROJECT REPORT**

**EC-104: Digital Logic Design**

## **Project Submitted By:**

Sarjan Jain : 13116034

Kandikunta Achut : 13116035

Kartik Patel : 13116036

K. Nagadeep : 13116037

Kumar Parimal : 13116038

Class: B. Tech. ECE 1<sup>st</sup> Year

# PROJECT STATEMENT

It converts serial bytes it receives into parallel data for outbound transmission.

**Design a circuit to take 16 bit serial data as input and output it in parallel form.**

# INDEX

## ☐ **Concept**

- Introduction
- Basic Concept
- Approach


## ☐ **Design**

- FSM Diagram
- VHDL Code
- Simulation

## ☐ **Summary**
 
# Introduction

- Takes 16-bit serial Input and convert it to parallel 16-bit form
- For transmission, UART protocol wraps 16-bit data with start and stop bit
- Optional parity bit is included just before stop bit
- For reception, first start bit is detected and based on the input clock serial data is sampled and converted to parallel form.



# Basic Concept

- When data is ready, transmitter sends “Start bit” to alert Receiver
- After that individual bits of the data is sent in serial with LSB first
- Receiver continuously receives serial bits with clock and convert them in parallel form
- When all data is sent a stop bit is sent by transmitter thereby signalling receiver to remain in “Start Bit Detection” state
- Optional parity check is also possible by adding parity bit just before last bit

# Basic Concept(Contd.)

- Start bit detection and validation
  - High to Low transition indicates a start bit.
  - Start bit validated if Receiver input is low during mid bit sampling
- A valid stop bit is HIGH when the stop bit is sampled

# Approach

- Assumption made:
  - Clock input is available which is 16 times defined baud rate
- First, Finite State Machine (FSM) diagrams are prepared before designing a logic in VHDL
- VHDL code is written and checked for syntax error
- Simulation carried out.


# Approach(Contd.)

- We have made Entity named CLK16 which converts given CLK input to 16 times CLK Rate. Here CLK input is in fact output of Baud Generator.
- We have made Entity named UART\_Receiver with 6 ports with 3 input and 3 Output Ports. One of the Output port is 16-bit data bus which is our parallel output.
- At first receiver needs Start Bit. After successful sampling of Start Bit, receiver will sample every further inputs with counting up to 16.
- At 17th count, receiver takes SER\_IN as Parity bit and checks for validation.
- If validated than it will transmit data to data bus. Else it will transmit '0' with Error='1'.



# Design

## FSM Diagram

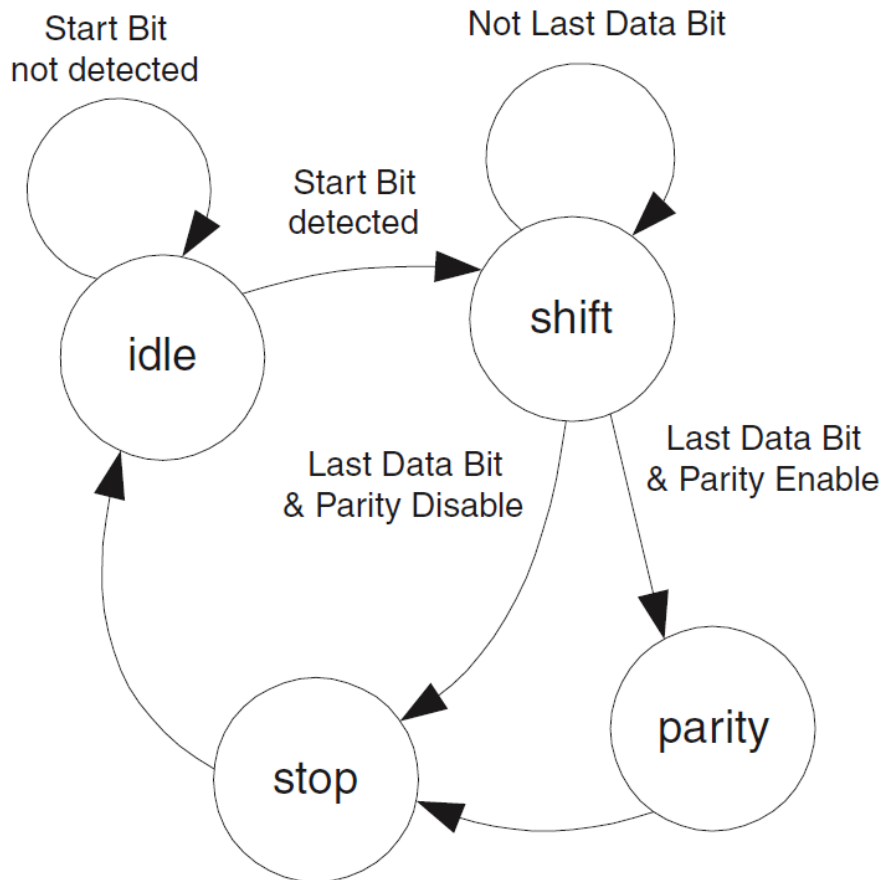

### Idle:


- Reset Button will reset machine to this state.
- In this state, receiver is waiting for SER\_IN to go from high to low i.e. start bit. After successful detection, it will shift to <shift> state.

### Shift:

- When Receiver is in this state, it waits for 1 clock cycle for each data bit to shift.
- After last Data bit is shifted in the receiver will switch to <parity> state if parity is enabled.
- Otherwise it will switch to <stop> state

# Design

## FSM Diagram

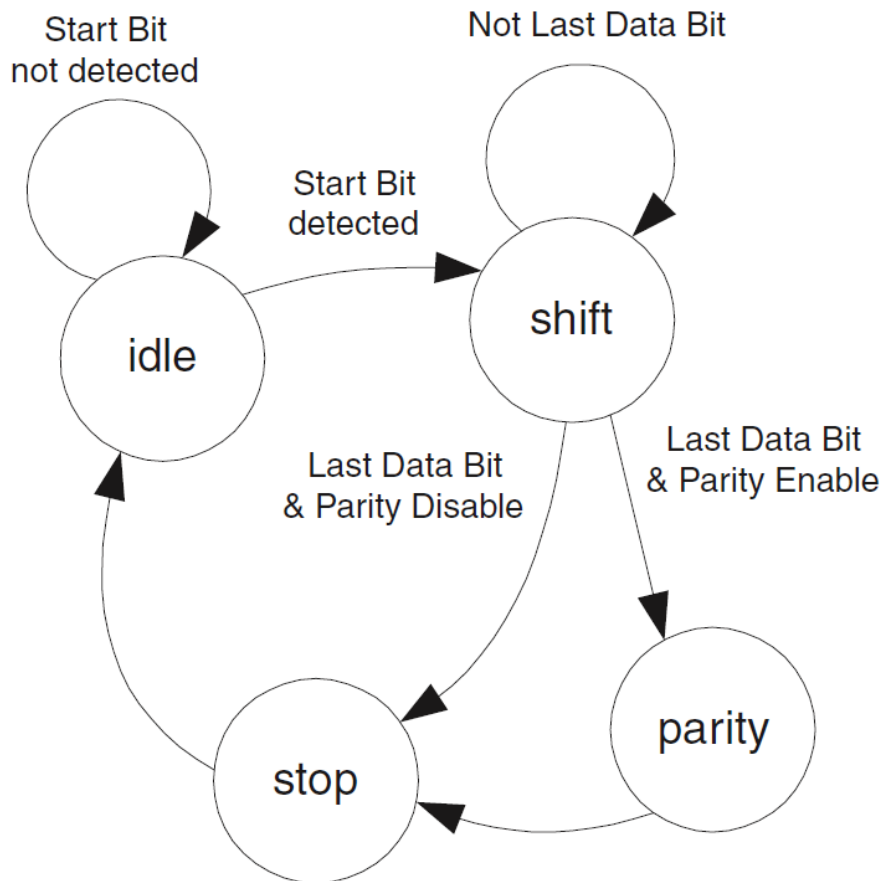

### Parity:

- When the FSM is in this state, it waits for next clock cycle and then samples parity bit.
- Once it is sampled it will switch to <stop> set.

### Stop:

- FSM will wait for 1 clock cycle and then samples the stop bit.
- The FSM switches back to <idle> state after the Stop bit sampling

# VHDL Code

## Entity Declaration for CLK16

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity CLK16 is
port (CLK : in std_logic;
      enable: in std_logic:='0';
      CLK16x : out std_logic := '0');
end CLK16;

architecture Behavioral of CLK16 is
signal currentCLK16x : std_logic := '1';
signal count : integer := 16;
```

### Ports Required:

- **CLK**: Clock input
- **CLK16x** : Output Port which changes values at every 16 counts. This is input for Receiver

# VHDL Code

## Architecture Block of CLK16

```
begin
process (CLK, enable)
begin
    if enable='1' then
        if Rising_edge (CLK) then
            if count=16 then
                currentCLK16x <= not currentCLK16x;
                CLK16x<=currentCLK16x;
            end if;
            count <= count-1;
            if count=0 then
                count<=16;
            end if;
        end if;
    end if;
end process;
end Behavioral;
```

# VHDL Code

## Entity Declaration

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
entity UART_Receiver is
port (SER_IN : in std_logic := '1';
      RESET : in std_logic;
      OUT16O : out std_logic_vector (15 downto 0) := (others=>'0');
      CLK : in std_logic;
      statusOUT : out std_logic := '0';
      ERROR: out std_logic := '0');
end UART_Receiver;
```

### Ports Required:

- **CLK**: Clock input for UART. Which is defined Baud rate.
- **RESET**: Asynchronous RESET Signal
- **SER\_IN**: Serial bit stream received by unit
- **ERROR**: Output goes '1' for Parity Error or Not getting Stop Bit after 16-bit
- **statusOUT**: Shows current status. For busy condition gives output '1'
- **OUT16O**: Output Bit vector in parallel form

# VHDL Code

## Architecture Block of UART\_Receiver

```
architecture Behavioral of UART_Receiver is
signal status : std_logic := '0';
signal par : std_logic := '0';
signal OUT16 : std_logic_vector(15 downto 0) := (others=>'0');
signal CLK16x : std_logic;
signal count : integer := 0;
component CLK16
    port (CLK: in std_logic;
          enable: in std_logic:= '0';
          CLK16x: out std_logic);
end component;
begin
    CLKP : CLK16 port map (CLK, status, CLK16x);
    pmain : process (RESET, SER_IN, CLK16x, CLK)
    begin
        if RESET='1' then
            OUT16O <= x"0000";
            OUT16 <= x"0000";
            ERROR <= '0';
            count<=0;
            par<='0';
            status<='0';
            statusOUT <= '0';
```



Reset Block

# VHDL Code

## Start Bit to Parity bit Sampling

```
elsif CLK16x'event and CLK16x='1' then
  if status='0' and SER_IN='0' then
    status<='1';
    statusOUT <= '1';
    count <=0;
```

Getting Start Bit

```
elsif status='1' and count<16 then
  count <= count+1;
  OUT16 <= OUT16(14 downto 0) & SER_IN;
```

Counting up and  
Shifting one bit to right until  
count reached to 16

```
  if SER_IN='1' then
    par <= not par;    --EVEN PARITY
  end if;
```

Update Parity if  
Input is '1'

```
elsif count=16 and status='1' then
  count<=17;
  if SER_IN=(not par) then
    ERROR <= '1';
    OUT16 <= x"0000";
  end if;
```

Check parity at  
last input i.e.  
count=16


# VHDL Code

## Sampling Stop bit and shift to IDLE state


```
elsif count=17 and SER_IN='1' and status='1' then
    --at 17th count, check for SER_IN=1 for IDLE and reset
    OUT160 <= OUT16;
    ERROR <= '0';
    status<='0';
    statusOUT<='0';
end if;
elsif count=17 and SER_IN='0' and status='1' then
    OUT160 <= x"0000";
    ERROR <='1';
    status<='0';
    statusOUT<='0';
end if;
end process;
end Behavioral;
```




# RTL Schematic : Block Diagram

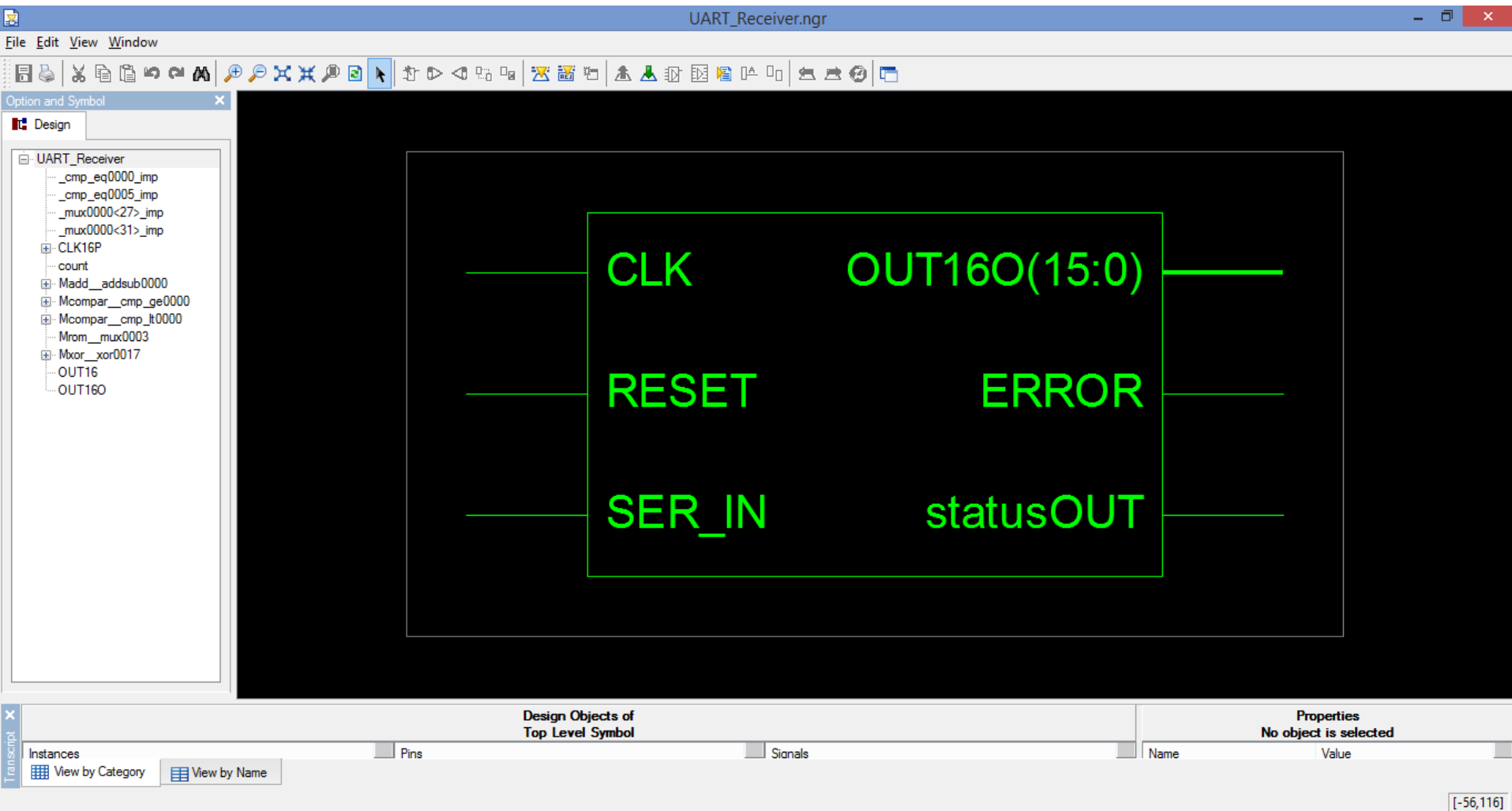


# RTL Schematic : Inside Block Pg. 1

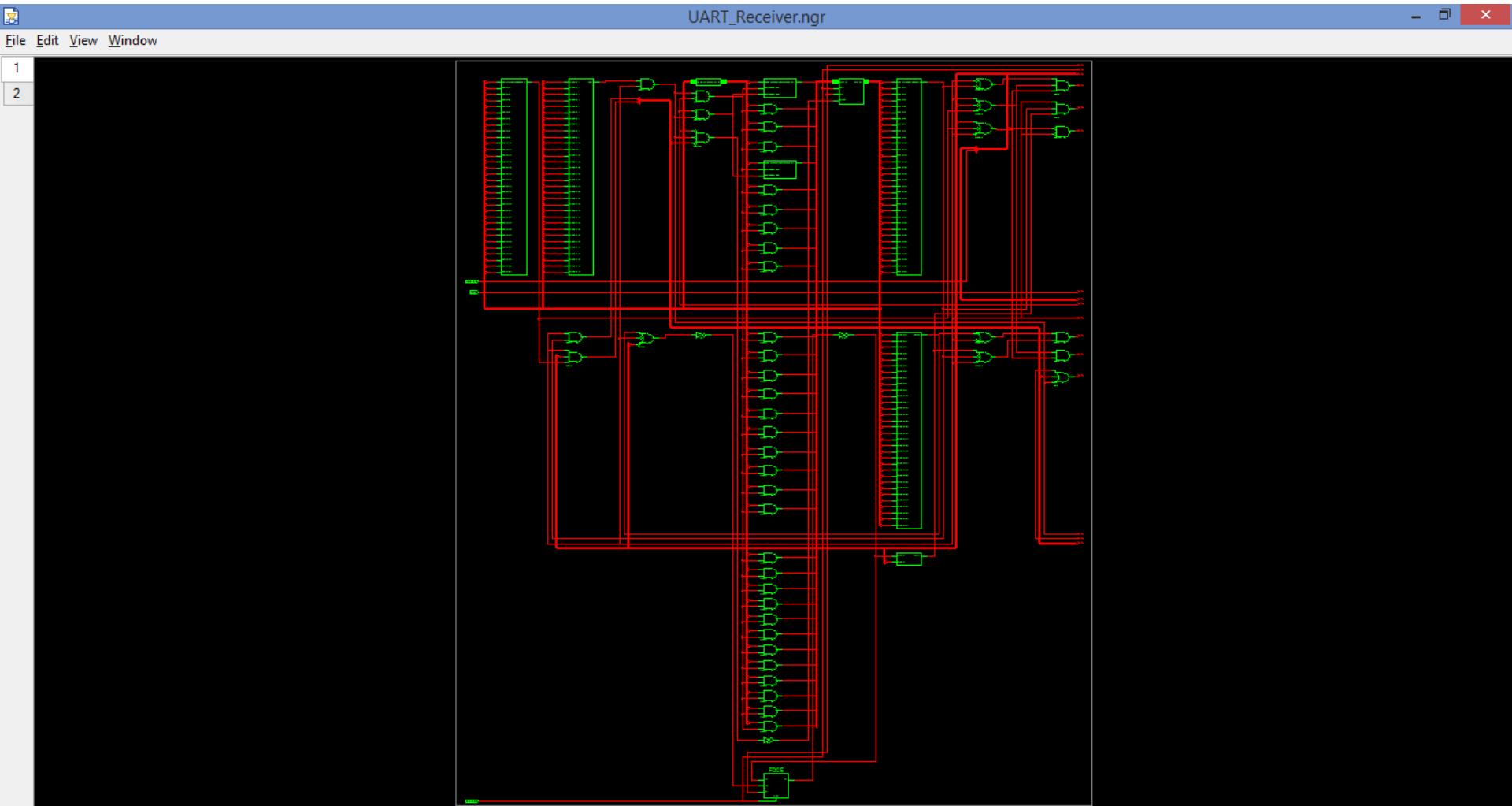

# RTL Schematic : Inside Block Pg. 2

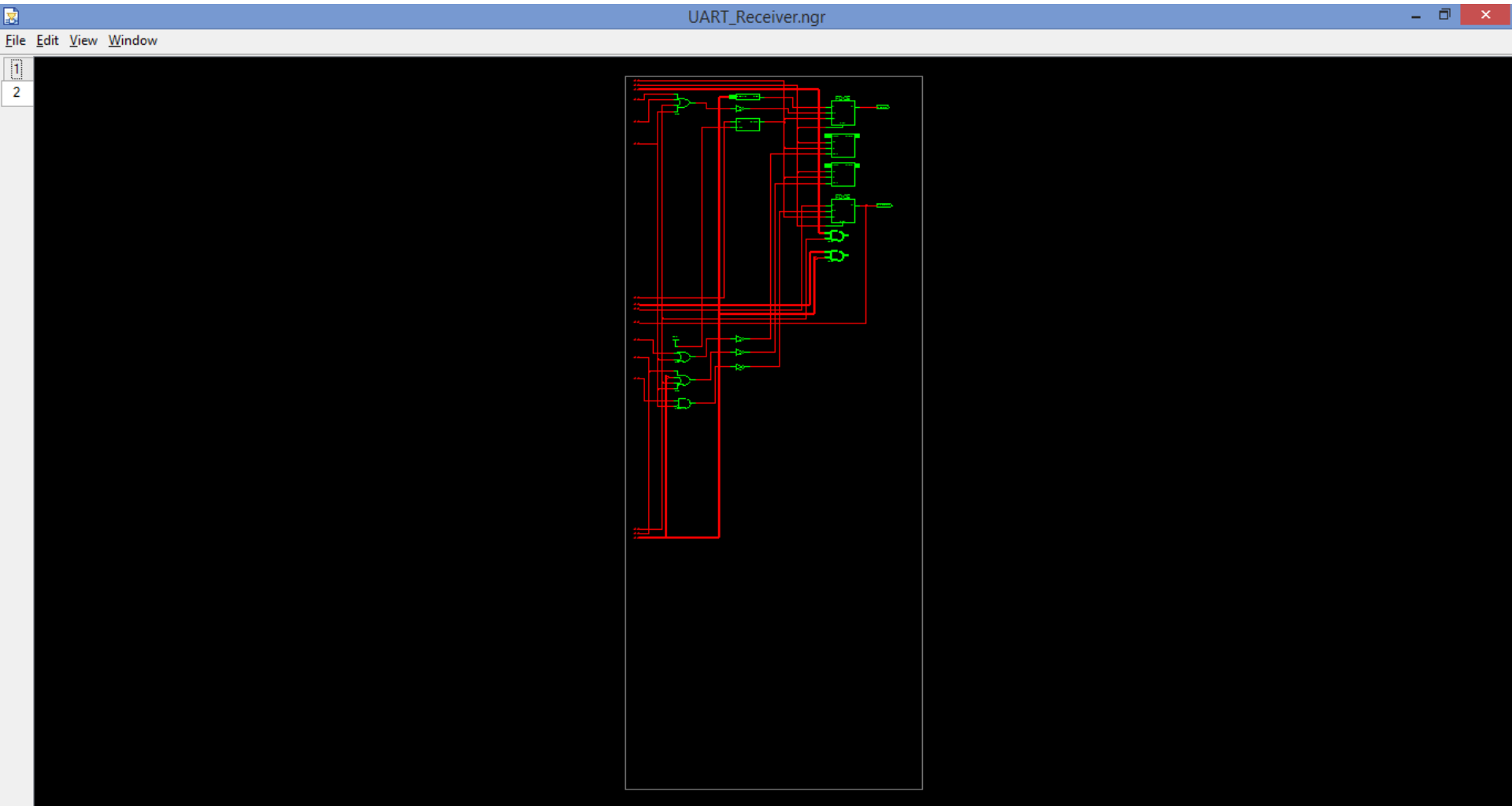

# Simulation Results

 

For simulation Purpose, we have used 2 times baud rate as Clock

# Summary

- UART Receiver is designed using VHDL and tested successfully on test bench simulation.
- Here clock cycle can be replaced by Baud Rate Pulses generated by Baud Rate Generator to accurately synchronise with Transmitter.

# Thank you